



INSTITUTO POLITÉCNICO NACIONAL

ESCUELA SUPERIOR DE COMPUTO

Std Logic Arith & Unsigned

Practica 7

Materia:

Arquitectura de computadoras

Profesor:

Castillo Cabrera Gelacio

Alumno:

Cortés Piña Oziel


Grupo:

3CM12

INSTITUTO POLITÉCNICO NACIONAL



Simulación en GHDL y GTLWAVE

 

```

make[1]: se sale del directorio '/home/oz/docs/school/ESCOM/p
make simulate
make[1]: se entra en el directorio '/home/oz/docs/school/ESCO
ghdl -r -fsynopsys test --vcd=sim.vcd
../../src/synopsys/std_logic_arith.vhdl:255:20:@0ms:(assertio
../../src/synopsys/std_logic_arith.vhdl:255:20:@0ms:(assertio
gtkwave sim.vcd --rcvar 'fontname_waves Monospac 22' --rcvar

GTKWave Analyzer v3.3.109 (w)1999-2020 BSI

RCVAR   | 'fontname_waves Monospac 22' FOUND
RCVAR   | 'fontname_signals Monospace 22' FOUND
[0] start time.
[120000000] end time.
^Cmake[1]: *** [Makefile:11: simulate] Interrupción
make: *** [Makefile:7: default] Interrupción

x 7 » m
make validate
make[1]: se entra en el directorio '/home/oz/docs/school/ESCOM/periods/6/arqui/rep
ghdl -s -fsynopsys *.vhdL
make[1]: se sale del directorio '/home/oz/docs/school/ESCOM/periods/6/arqui/rep/7
make build
make[1]: se entra en el directorio '/home/oz/docs/school/ESCOM/periods/6/arqui/rep
ghdl -a -fsynopsys *.vhdL
cat work-obj*
v 4
file . "test.vhdl" "4b01efa20dc739e56209bb321f4a474d0b1df0f2" "20210928220954.143"
  entity test at 1( 0) + 0 on 25;
  architecture arch of test at 9( 133) + 0 on 26;
file . "adder8bit.vhdl" "612e4c254875d95f54daf17d4cf4826d6e01b40c" "20210928220954
  entity adder8bit at 1( 0) + 0 on 23;
  architecture adder8bit_arch of adder8bit at 15( 273) + 0 on 24;
ghdl -e -fsynopsys test
make[1]: se sale del directorio '/home/oz/docs/school/ESCOM/periods/6/arqui/rep/7
make simulate
make[1]: se entra en el directorio '/home/oz/docs/school/ESCOM/periods/6/arqui/rep
ghdl -r -fsynopsys test --vcd=sim.vcd
../../src/synopsys/std_logic_arith.vhdl:255:20:@0ms:(assertion warning): There is
../../src/synopsys/std_logic_arith.vhdl:255:20:@0ms:(assertion warning): There is
gtkwave sim.vcd --rcvar 'fontname_waves Monospac 22' --rcvar 'fontname_signals Mon

GTKWave Analyzer v3.3.109 (w)1999-2020 BSI

RCVAR   | 'fontname_waves Monospac 22' FOUND
RCVAR   | 'fontname_signals Monospace 22' FOUND
[0] start time.
[120000000] end time.

```

Código VHDL

Adder8bit

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;

entity adder8bit is
    port(
        sel: in      std_logic;
        anum: in      unsigned(7 downto 0);
        bnum: in      unsigned(7 downto 0);
        sum: out      unsigned(7 downto 0)
    );
end adder8bit;

architecture adder8bit_arch of adder8bit is
begin
    sum <= anum + bnum when sel = '0'
        else anum - bnum;
end adder8bit_arch;
```

Test

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;

entity test is
end test;

architecture arch of test is
    component adder8bit is
        port(
            sel: in      std_logic;
            anum: in      unsigned(7 downto 0);
            bnum: in      unsigned(7 downto 0);
            sum: out      unsigned(7 downto 0)
        );
    end component;
    signal sel: std_logic;
    signal anum: unsigned(7 downto 0);
    signal bnum: unsigned(7 downto 0);
    signal sum: unsigned(7 downto 0);
begin
    adder: adder8bit port map( sel => sel, anum => anum, bnum => bnum, sum => sum );
    process begin
        sel <= '0';
        anum <= "00000011";
        bnum <= "00000100";
        wait for 20 ns;
        anum <= "01000000";
        bnum <= "01000010";
        wait for 20 ns;
        anum <= "10000001";
        bnum <= "10000000";
    end process;
```

```

        wait for 20 ns;
        sel <= '1';
        anum <= "00000011";
        bnum <= "00000100";
        wait for 20 ns;
        anum <= "01000000";
        bnum <= "01000010";
        wait for 20 ns;
        anum <= "10000001";
        bnum <= "10000000";
        wait for 20 ns;
        wait;
    end process;
end arch;

```

Análisis de vectores

Practica 6

Vectores de entrada

A		B	
Binario	Hexadecimal	Binario	Hexadecimal
00000011	3	00000100	4
01000000	40	01000010	42
10000001	81	10000000	80

Valores de salida

A		B		Selector		
Binario	Hexa	Binario	Hexa	Binario	Binario	Hexa
00000011	3	00000100	4	0	00000111	7
01000000	40	01000010	42	0	00000000	0
10000001	81	10000000	80	0	00000000	0
00000011	3	00000100	4	1	11111111	FF
01000000	40	01000010	42	1	11111110	FE
10000001	81	10000000	80	1	00000001	1

Practica 7

Vectores de entrada

A		B	
Binario	Hexadecimal	Binario	Hexadecimal
00000011	3	00000100	4
01000000	40	01000010	42
10000001	81	10000000	80

Valores de salida

A		B		Selector		
Binario	Hexa	Binario	Hexa	Binario	Binario	Hexa
00000011	3	00000100	4	0	00000111	7
01000000	40	01000010	42	0	00000000	82
10000001	81	10000000	80	0	00000000	01
00000011	3	00000100	4	1	11111111	FF
01000000	40	01000010	42	1	11111110	FE
10000001	81	10000000	80	1	00000001	1

Conclusión

La biblioteca de arith en VHDL permite realizar circuitos más fáciles y ahorra mucho tiempo más sin en-cambio arroja valores distintos al momento de realizar las operaciones de suma y resta haciendo que se aproveche el número a sumarse y restarse a diferencia del circuito anterior en el que teníamos desbordes. Pareciera que usa los positivos y negativos a su favor del número para representarlo.